

**Bachelor of Computer Application (B.C.A.) Semester-III (C.B.S.) Examination****DIGITAL ELECTRONICS-I****Paper—VI**

Time : Three Hours]

[Maximum Marks : 50

**N.B. :—** (1) All questions are compulsory and carry equal marks.

(2) Draw a well labelled diagram wherever necessary.

**EITHER**

1. (a) What is number system ? Explain binary, octal and hexadecimal number system with example. 5

(b) Do as directed :

(i)  $(134F)_{16} = (?)_2$

(ii)  $(3467)_8 = (?)_{10}$  5

**OR**

(c) What is parity ? What are its types ? What are its advantages ? 5

(d) What is Excess-3 code ? Perform the following addition using excess-3 code :

(i)  $22 + 44$

(ii)  $36 + 41$ . 5

**EITHER**

2. (a) How are positive and negative numbers separated in binary ? Explain with example. 5

(b) What is 1's complement of a number ? Perform the following subtraction using 1's complement method :

$(10110)_2 - (1011)_2$  5

**OR**

(c) What are the different rules for binary addition ? Perform the following binary addition :

(i)  $(1010)_2 + (111)_2$

(ii)  $(1111)_2 + (1000)_2$  5

(d) Explain the following with example :

(i) Underflow of data

(ii) Range of data

(iii) Overflow of data. 5

**EITHER**

3. (a) Explain AND, OR and NOT gate with their truth table. 5

(b) Explain how NOR gate can be used to construct :

(i) AND gate

(ii) OR gate

(iii) NOT gate. 5

**OR**

(c) Explain the construction and working of Ex-OR gate using basic gates. 5

(d) Why NAND gate is called universal gate ? Explain. 5

**EITHER**

4. (a) State and prove De-Morgan's theorem with truth table. 5
- (b) What is K-map ? Explain the following terms related to K-map :
- (i) SOP
  - (ii) POS
  - (iii) Quad
  - (iv) Octate
  - (v) Pair. 5

**OR**

- (c) State and prove :
- (i) AND law
  - (ii) OR law
  - (iii) NOT law. 5
- (d) Simplify the following equation using K-map :
- $$Y = \sum m(0, 2, 4, 6, 9, 11, 13)$$
- draw the logic diagram for simplified equation. 5
5. Attempt all :
- (a) What is ASCII code ? What are its advantages ? 2½
  - (b) Find the 2's complement of :
    - (i)  $(1000)_2$
    - (ii)  $(1111)_2$  2½  - (c) Draw the logic diagram of Ex-NOR gate and give its truth table. 2½
  - (d) Prove :
- $$(A + \bar{A} B) = (A + B) \quad 2\frac{1}{2}$$