

Faculty of Engineering & Technology
Eighth Semester B.E. (Industrial Electronics)
Examination

DESIGN OF ELECTRONIC CIRCUITS
Sections—A & B

Time : 3 Hours]

[Maximum Marks : 80

INSTRUCTIONS TO CANDIDATES

- (1) All questions carry marks as indicated.
- (2) Answer **TWO** questions from Section A and **TWO** questions from Section B.
- (3) Due credit will be given to neatness and adequate dimensions.
- (4) Assume suitable data wherever necessary.
- (5) Illustrate your answers wherever necessary with the help of neat sketches.
- (6) Use of Non-programmable calculator is permitted.

SECTION—A

1. (a) Design an unregulated DC power supply with capacitor filter arrangement is used to supply 400 mA current to a circuit operating at 12 V DC. The ckt. can tolerate 3 V peak to peak ripple voltage. Assume supply frequency 50 Hz.

8

(b) Design a step-up type SMPS to provide $V_o = 25 \text{ V}$ at 1.5 A . The unregulated input is 12 V . Time period of switching regulator is $40 \mu\text{sec}$. The ON voltage of diode and transistor is 1 V each. The transistor used as switching time $1.2 \mu\text{ sec}$. $I_{\text{Coff}} = 10 \text{ mA}$. If the output ripple is to be limited to 300 mV (P—P) and resistor is $35 \text{ m}\Omega$ effective series resistance, find the value of L and C . Assume $V_{\text{ref}} = 1.4 \text{ V}$. 12

2. (a) Design a Series Voltage Regulator to give $V_o = 12 \text{ V}$ at 350 mA . If $V_i = 26 \text{ V} \pm 15\%$ at no load, $r_o = 3 \Omega$, $h_{fe1} = 40$, $h_{fe2} = 100$, find out the values of S_v and R_o . 12

(b) Write a short note on class-C tuned amplifier with neat sketch. 8

3. Design Bootstrapped emitter follower ckt. to give $V_o = 0.3 \text{ V}$ peak if source voltage $V_s = 0.5 \text{ V}$ peak. Assume $V_{cc} = 12 \text{ V}$, $I_c = 0.7 \text{ mA}$. Capacitively coupled $R_L = 3 \text{ K}$. Transistor used has $h_{fe} = 100$. Source resistance of signal generator is 60 K . 20

4. (a) Design a 4 bit DAC using binary weighted resistance and reference voltage of 10 V . Find the output voltage if the binary input is 0011 . 12

(b) Write a short note on Sample and Hold Circuit. 8

SECTION—B

5. (a) Differentiate between Active and Passive Filters. 6

(b) Design a Butterworth filter which will give 2 dB attenuation at 1 kHz and 20 dB at 8 kHz . 14

6. Derive the expression for frequency of oscillation and figure of merit for Colpitt's oscillator. 20

7. (a) Differentiate between Combinational Logic and Sequential Logic. 5

(b) Design a ckt. using PLA so as to implement BCD to excess 3 code conversion. 15

8. Write short notes on (any **TWO**) :—

(i) Chopper using transistors

(ii) Algorithmic State machine

(iii) Voltage controlled oscillator (VCO)

(iv) Converter for DC motors. 20