

**Faculty of Engineering & Technology**  
**Eighth Semester B.E. (Power Electronics) Examination**  
**DESIGN OF POWER ELECTRONIC CIRCUITS**  
**Sections—A & B**

Time : 3 Hours]

[Maximum Marks : 80

**INSTRUCTIONS TO CANDIDATES**

- (1) All questions carry marks as indicated.
- (2) Answer **TWO** questions from Section A and **TWO** questions from Section B.
- (3) Assume suitable data wherever necessary.
- (4) Illustrate your answers wherever necessary with the help of neat sketches.
- (5) Use of non-programmable electronic calculator is permitted.

**SECTION—A**

1. (a) What are the advantages and disadvantages of switch mode power supply over the conventional power supply ? 5
- (b) Design the SMPS with the following specifications :

$$V_o = 10 \text{ V}$$

$$I_{Lmax} = 1 \text{ Amp}$$

$$V_i = 20 \pm 15\%$$

$$\Delta V_o = 20 \text{ mV}$$

$$\text{Switching frequency} = 25 \text{ kHz}$$

Derive the design equations. 15

2. (a) Design of regulator using IC 723 for the output voltage of 5 Volts.

What is line regulation, load regulation for the regulator circuit ? 12

- (b) Draw the circuit of 555 IC timer as a monostable multivibrator and sketch the waveforms of trigger pulse voltage and output voltage. 8

3. (a) Design Colpitt's Oscillator for an oscillating frequency of 150 kHz.

$$\text{Assume } V_{CC} = 18 \text{ V}$$

$$\text{Gain of an amplifier, } A_v = 10 \quad 8$$

- (b) Design a class-B audio power amplifier to deliver an output power of 5 watts to a load of  $10 \Omega$  resistance.

$$\text{Assume, } V_{CC} = 12 \text{ V}$$

$$h_{FE} \text{ for a power transistor} = 25 \quad 12$$

4. (a) The SCR has forward breakover voltage of 150 V when gate current of 2 mA flows in the gate circuit. When a sinusoidal voltage of

400 V rms is applied to it, find the average value of the output voltage.

(Draw necessary waveform) 8

(b) Write technical notes on (any **TWO**) :—

(i) Over voltage protection in linear regulators 6

(ii) Emitter Follower Regulator Design. 6

(iii) Design of LC transistorised oscillators. 6

### SECTION—B

5. (a) Explain the working of multiphase chopper with waveforms. 6

(b) A highly inductive load is controlled by the chopper shown in Fig. Q. 5(b) requires an average current of 400 Amp with a peak value of 450 Amp.

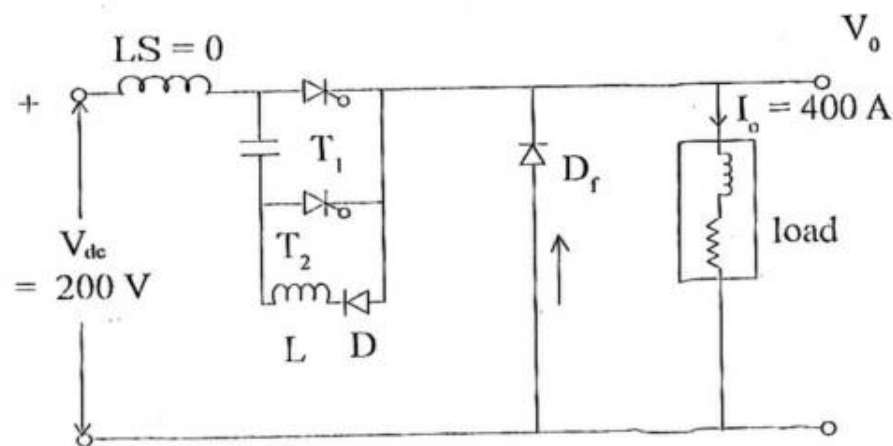


Fig. Q. 5(b)

Input dc voltage = 200 V

Chopping frequency = 500 Hz and

Turn-off time of SCR = 20  $\mu$ s. If the peak current through the SCR is limited to 1.71 m, determine the sizes of L and C and also find the minimum and maximum values of output voltages. 14

6. (a) State the design criteria for designing a pulse transformer for triggering SCRs in a 1  $\phi$  converter. Discuss the conditions under which input pulse is faithfully transmitted or is transmitted in the form of exponentially delaying pulse. 12

(b) Design a UJT triggering circuit for 1  $\phi$  full wave fully controlled converter to deliver output voltage from 0—220 V. The input supply is 230 V<sub>rms</sub>. 8

7. (a) A full bridge bipolar PWM inverter is operated from a 240 V battery and is driving an RL load. Find out the following if the modulation index  $m = 0.8$  :

(i) Total RMS output voltage

(ii) Fundamental output voltage

(iii) Distortion factor

(iv) Harmonic factor

(v) Gain of the inverter. 13

- (b) A series inverter has following parameters :  
inductance  $L = 12 \text{ mH}$ ,  $C = 0.1 \text{ } \mu\text{F}$ , load resistor  
 $R = 100 \text{ } \Omega$  and  $T_{\text{off}} = 0.3 \text{ ms}$ .

Determine :—

- (i) the frequency of the output voltage
  - (ii) the attenuation factor. 7
8. (a) Design the control circuit of a 3 ph induction motor, using volt-frequency control. 10
- (b) Give the design of OTT filter for a square-wave inverter. 10