

**Bachelor of Science (B.Sc.) Semester—IV (C.B.S.) Examination**

**ELECTRONICS**

**(Analogue & Digital Techniques)**

**Compulsory Paper—1**

Time : Three Hours]

[Maximum Marks : 50

**N.B. :—** (1) **ALL** questions are compulsory and carry equal marks.

(2) Draw neat and well labelled diagrams wherever necessary.

**EITHER**

1. (A) State and derive Barkhausen criteria for oscillations. Explain working of phase-shift oscillator using OP-AMP. An RC oscillator with OP-AMP has three RC sections in the feedback loop with  $R = 22\text{ k}\Omega$  and  $C = 10\text{ pF}$ . Calculate the frequency of its output. 4+4+2

**OR**

- (B) Explain the equivalent circuit of a Piezoelectric crystal. With a neat circuit diagram, explain the construction and working of NOT gate based crystal oscillator. State advantages of crystal oscillator. 4+4+2

**EITHER**

2. (A) Explain construction and working of OP-AMP based Astable multivibrator. Derive the expression for the frequency of its output. Calculate the frequency of output of an astable multivibrator having  $R_1 = 35\text{ k}\Omega$ ,  $R_2 = 30\text{ k}\Omega$ ,  $R = 50\text{ k}\Omega$  and  $C = 0.01\text{ }\mu\text{F}$ . 8+2

**OR**

- (B) What is the need of Sample and Hold Circuit in electronic instrumentation ? Explain any one type of S/H circuit. Explain construction and working of an Instrumentation amplifier with three OP-AMPs. 2+4+4

**EITHER**

3. (A) With respect to a DAC, define the following :  
(a) Resolution  
(b) Accuracy.  
Explain working of R – 2R type DAC. What are its advantages (any two) ? 2+6+2

**OR**

(B) Logic levels for a 4-bit R – 2R ladder are 1 = 5 V and 0 = 0 V. Calculate :

- (i) Range
- (ii) Resolution
- (iii) Output voltage for (a) 1010 and (b) 0100.

State any two applications of DAC.

2+2+2+2+2

**EITHER**

4. (A) State and explain Sampling Theorem. With a neat circuit diagram, explain the construction and working of 3-bit flash type ADC. 3+7

**OR**

(B) Explain the Algorithm of a successive approximation ADC. Draw the block diagram of a successive approximation ADC and explain its working. 5+5

5. Answer any **TEN** :

- (A) State any two factors affecting the stability of output frequency of an oscillator.
- (B) Draw the circuit symbol of an oscillator.
- (C) Why are LC oscillators used at high frequencies only ?
- (D) State the type of feedback used in a monostable multivibrator.
- (E) Why do we use CMOS switches in a S/H circuit ?
- (F) State any two applications of Data Acquisition System.
- (G) What is the need of DAC in electronic instrumentation system ?
- (H) State the principle of Dual bias DAC.
- (I) Why is it useful to connect an OP-AMP at the output of a DAC ?
- (J) State two disadvantages of a single slope ADC.
- (K) What is quantisation error in ADC ?
- (L) What is the role of a comparator in ADC ?

1×10=10