

KNT/KW/16/5269

Bachelor of Computer Application (B.C.A.) Semester—IV (C.B.S.) Examination**DIGITAL ELECTRONICS-II****Paper—VI**

Time : Three Hours]

[Maximum Marks : 50

N.B. :— (1) **ALL** questions are compulsory and carry equal marks.

(2) Draw neat labelled diagrams wherever necessary.

EITHER

1. (a) Draw a 4 bit parallel adder circuit and explain its working. 5
- (b) Design a 8 : 1 multiplexer using 4 : 1 multiplexer. 5

OR

- (c) Draw a 4 bit binary subtractor and explain its working. 5
- (d) What is a decoder ? Design a 3 to 8 line decoder circuit using K-map. 5

EITHER

2. (a) Construct a clocked RSFF using only Nano gates and explain its working. 5
- (b) Explain the construction and working of mod-6 asynchronous counter. 5

OR

- (c) What is race around condition ? Explain the methods of avoiding race around condition. 5
- (d) Explain the construction and working of 3-bit synchronous counter. 5

EITHER

3. (a) Draw the block diagram of 8086. Explain. 5
- (b) Write an ALP to add series of 10 numbers. 5

OR

- (c) What are different addressing modes of 8086 ? Explain. 5
- (d) What are the different flags of 8086 ? Explain. 5

EITHER

4. (a) What do you mean by assembler directives ? Explain with suitable example. 5
- (b) What are the different transfer control instructions ? Explain. 5

OR

- (c) Write ALP to multiply two numbers. 5
- (d) Explain string manipulation instructions with example. 5
5. (a) Draw a full adder circuit and explain its working. 2½
- (b) Draw JKMSFF using only NAND gates and explain its working. 2½
- (c) What are the different interrupts of 8086 ? 2½
- (d) Write ALP to add two numbers stored in memory. 2½