

VKR/KS/13/3278/3613

Faculty of Engineering & Technology

Eighth Semester B.E. (Electrical)/Eighth Semester B.E.

P.T. (Electrical) Examination

POWER SEMICONDUCTOR BASED DRIVES

Sections—A & B

Time : Three Hours]

[Maximum Marks : 80

INSTRUCTIONS TO CANDIDATES

- (1) All questions carry marks as indicated.
- (2) Answer **THREE** questions from Section—A and **THREE** questions from Section—B.
- (3) Assume suitable data wherever necessary.
- (4) Illustrate your answers wherever necessary with the help of neat sketches.

SECTION—A

1. (a) A motor is used to drive a Hoist. Motor characteristics are given by :  
Quadrants I, II, and IV,  $T = 200 - 0.2 N \mu\text{-m}$   
Quadrants II, III, and IV,  $T = -200 - 0.2 N, \mu\text{-m}$

- (b) Draw a neat circuit diagram and explain the working of Self controlled synchronous motor drive using load commutated inverter. 6

- (a) What are the main features of stepper motor which are responsible for its widespread use. 7

- (b) Draw a block diagram and explain solar pump drive using battery. What are the advantages and disadvantages of using a battery in solar pump drive ? 6

- (a) Explain in brief 25 kV ac traction using transformer with tap changer. 7

- (b) Discuss the operation of dc traction using VSI Fed Induction motor drive. How composite braking is carried out ? 6

10. Write short notes :—

- (a) Brushless DC motor. 7
- (b) Cycloconverter fed synchronous motor drive. 7

where  $N$  is speed in rpm when hoist is loaded, the net load torque  $T_l = 100 \text{ N-m}$  and when it is unloaded, net load torque  $T_l = -80 \text{ N-m}$ . Obtain the equilibrium speeds for operations in all the four quadrants. 7

- (b) Explain how following speed transitions are carried out :—
- Increase in the speed in same direction.
  - Decrease in the speed in same direction.
  - Speed reversal. 6

2. (a) A 220 V, 1500 rpm, 50 A separately excited dc motor with armature resistance of 0.5 ohm, is fed from a 3-phase fully controlled converter. Available ac source has a line voltage of 440 V, 50 Hz. A star-delta connected transformer is used to feed the armature so that motor terminal voltage equals rated voltage when converter firing angle is zero.

- Calculate transformer turns ratio.
- Determine the firing angle when motor is running at  $-800 \text{ rpm}$  and twice the rated torque. 7

- (b) Draw a neat circuit diagram and explain the operation of chopper controlled dc drives. Also draw the necessary waveform. 6

- Draw a neat circuit diagram and explain the working of static Scherbius drive. 7
  - Briefly explain the working of current source inverter fed Induction motor drive. 6
- Explain in brief the steady state stability of motor-load system. 7
  - Draw a neat circuit diagram and explain the working of Fractional hp motors. 6
- Write short notes :—
  - Energy conservation in electrical drives. 7
  - Components of load torque. 7

### SECTION—B

- Describe a chopper controlled dc traction drive with composite braking. How is it ensured to minimise energy dissipation in dynamic braking. 7
  - Discuss 25 kV ac traction using thyristor converted with sequence control. Also draw the relevant waveforms and circuit diagram for the stage converter. 6
- Explain in brief the difference between run synchronous mode and self control mode for variable frequency control of synchronous motor. 7