

VKR/KS/13/3279/3557/3411

Faculty of Engineering & Technology
Eighth Semester B.E. (Electrical Engg.)/Power Engg./
Seventh Semester B.E. P.T. (Electrical)/Eighth
Semester B.E. (PEngg.) Examination
SWITCHGEAR AND PROTECTION
Sections—A & B

Time : Three Hours]

[Maximum Marks : 80

INSTRUCTIONS TO CANDIDATES

- (1) Answer **THREE** questions from Section A and **THREE** questions from Section B.
- (2) Assume suitable data wherever necessary.
- (3) Illustrate your answers wherever necessary with the help of neat sketches.
- (4) Use of slide rule, Drawing instruments and non-programmable calculator is permitted.

SECTION—A

1. (a) Explain in short :—
 - (i) What is meant by an external and an internal fault ?
2
 - (ii) Why are adjacent zones made to overlap ?
2

MNO—39178

1

(Contd.)

- (iii) Why speed of protection is important ? 2
 (iv) "Power systems are moving towards increasing complexity, demand and equally complex protection". Discuss. 2

(b) What is meant by back-up protection ? What is its necessity ? Explain its various types. 5

2. (a) Compare the time-current characteristics of inverse, very inverse and extremely inverse overcurrent relays ? Discuss their area of applications. 6

(b) What do you mean by TSM and PSM ?

The rating of an overcurrent relay is 5 A.
 PSM = 2, TSM = 0.3, CT ratio = 400/5, Fault current = 4000 A.

Determine the operating time of the relay. At TSM = 1, operating times at various PSM are :—

PSM	2	4	5	8	10	20
Operating time in seconds	10	5	4	3	2.8	2.4

7

3. (a) Explain how you provide directional feature to (i) impedance and (ii) reactance relay. 3

(b) Draw and explain the circuit connection of three reactance units used at a particular location for 3 zones of distance protection. 7

(c) In what way is distance protection superior to overcurrent protection for the protection of H.V. transmission lines ? 3

4. (a) Explain the need of directional relay. Derive torque equation from the phasor diagram. 6

(b) A 110 kV line of 35 km length is protected by impedance relay. The first stage of distance relay protects 80% of the line. Calculate the setting of impedance relay and draw the characteristic of line and the relay on R-X plane. Neglect the influence of arc resistance.

The line impedance is $(0.24 + j0.41) \Omega$ per conductor per km. CT ratio is 300/1 A and PT ratio is 110 kV/110 V. 7

5. Write short notes on (any TWO) :—

(i) Induction cup relay. 7

(ii) Directional overcurrent relay. 7

(iii) Underreach and overreach of distance relay. 7

SECTION—B

6. (a) Explain the various faults in induction motor and their remedies in short. 6

(b) A 3-phase 33 kV star connected alternator is to be protected using circulating current protection. The pilot wires are connected to the secondary windings of 100/5 ratio current transformer. The protective relay is adjusted to operate with an out of balance current of 1 Amp in the pilot wires. Determine the :

- (i) earthing resistance which will protect 90% of the winding and
- (ii) the % of the winding which would be protected if the earthing resistance is 15Ω .

8

7. (a) With a neat sketch, discuss the differential scheme for bus-zone protection. 5

(b) A 3-phase 60/11 kV star-delta connected transformer is provided by Merz-price protection system. The CTs on LT side have a ratio of 420/5 Amps. Show that the CTs on H.T. side will have a ratio of $70:5/\sqrt{3}$.

Draw circuit diagram. 8

8. (a) Explain static definite time over-current relay. 6

(b) Explain the duality between phase and amplitude comparator. 7

9. (a) Discuss the principle of an arc interruption in
(i) an oil circuit breaker and
(ii) air blast circuit breaker. 5

(b) Explain the terms :—

- (i) restriking voltage
- (ii) recovery voltage and
- (iii) RRRV.

Derive an expression for the restriking voltage in terms of system voltage. 8

10. (a) An 11 kV, 50 Hz alternator is connected to a system which has inductance and capacitance per phase of 10 mH and $0.01 \mu\text{F}$ respectively. Determine :

- (i) the maximum voltage across the breaker contacts.
- (ii) frequency of transient oscillation
- (iii) the average RRRV and
- (iv) Maximum RRRV. 6

(b) Explain SF_6 circuit breaker. 7