

9. (a) Explain addressing modes of  $\mu p$  8085. 4  
 (b) Explain Architecture of 8085 in detail. 9

**OR**

10. (a) Explain the following instructions :  
 (i) STAX B  
 (ii) Push B  
 (iii) DAD rp  
 (iv) LXI H, address. 8  
 (b) Explain the following pins of  $\mu p$  8085 :  
 (i) Ready  
 (ii) HOLD  
 (iii) HLDA. 5
11. (a) Write an assembly language program to arrange 10 bytes stored from 8000 H in descending order and store in memory locations starting from C000H. 8  
 (b) Explain bit format of SIM and RIM instruction in 8085. 5

**OR**

12. (a) Draw timing diagram of instruction SHLD 5000 H. 6  
 (b) Explain hardware interrupt structure of  $\mu p$  8085. 7

**Faculty of Engineering & Technology**  
**Third Semester B.E. (Information Technology)**  
**(C.B.S.) Examination**

**DIGITAL ELECTRONICS & FUNDAMENTAL OF**  
**MICROPROCESSOR**

**Paper—IV**

Time—Three Hours]

[Maximum Marks—80

**INSTRUCTIONS TO CANDIDATES**

- (1) All questions carry marks as indicated.
- (2) Answer **SIX** questions.
- (3) Assume suitable data wherever necessary.
- (4) Illustrate your answers wherever necessary with the help of neat sketches.

1. (a) Convert the following :  
 (i)  $(596432.896)_D = ( ? )_B$   
 (ii)  $(10110101.0101)_G = ( ? )_B$   
 (iii)  $(ABCD.EF)_H = ( ? )_8$   
 (iv)  $(7654.32)_8 = ( ? )_D$  8  
 (b) Draw NAND and EX-OR gates and write their truth tables. 5

**OR**

2. (a) Write short note on ASCII code. 5  
 (b) State law of complementation in boolean algebra. 2  
 (c) Simplify the following function using boolean algebra :  
 (i)  $f(A, B, C) = ABC + AB\bar{C} + A\bar{B}$   
 (ii)  $f(A, B, C, D) = ACD + \bar{A}CD + AB\bar{C} + ABC$   
 (iii)  $f(A, B, C, D) = \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}D + ABCD + \bar{A}\bar{B}C\bar{D}$  6
3. (a) Simplify using K-map :  
 (i)  $f(A, B, C, D) = \sum m(0, 4, 5, 8, 9, 12, 13, 15) + d(1, 6, 14)$   
 (ii)  $f(A, B, C, D) = \pi M(0, 4, 7, 13, 15)$  6  
 (b) Express given function in standard SOP and standard POS forms :  
 $f(W, X, Y, Z) = \bar{W}\bar{X}Z + WX\bar{Y}Z + WY\bar{Z}$ . 6  
 (c) Explain Min and Max terms. 2

**OR**

4. (a) Simplify using K-map and implement using NAND gates only :  
 $f(A, B, C, D) = \sum m(0, 4, 6, 8, 10, 12, 14)$ . 7  
 (b) By finding standard POS form of :  
 $f(A, B, C, D) = \bar{A}\bar{B}C\bar{D} + AB\bar{C} + \bar{A}BCD + ACD$   
 Write truth table of the function. 7


5. (a) Explain working of BCD adder circuit. 7  
 (b) Implement following functions using suitable decoders and logic gates :  
 (i)  $f_1(A, B, C) = \sum m(0, 2, 3, 6, 7)$   
 (ii)  $f_2(A, B, C) = \sum m(1, 4, 5, 7)$ . 6

**OR**

6. (a) Implement the given function using 8 : 1 MUX :  
 $f(W, X, Y, Z) = \Pi M(0, 4, 7, 11, 12, 15)$ . 7  
 (b) Design full subtractor circuit using logic gates. 6
7. (a) Explain working of SR flip flop using NAND gates only. 6  
 (b) What is race around condition in JK flip flop ? 4  
 (c) What is difference between synchronous and asynchronous counters ? 4

**OR**

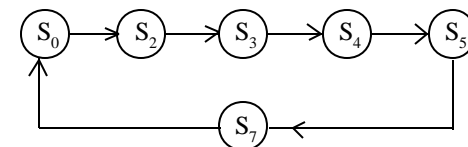8. (a) Design Mod-6 synchronous counter using D flip flops. 8



- (b) Convert the following :  
 (i) T to D flip flop  
 (ii) JK to SR flip flop. 6