

## First Semester B. Sc. Examination

## ELECTRONICS

## Paper - II

## (Fundamentals of Digital Electronics)

Time : Three Hours ]

[ Max. Marks : 50

- N. B. : (1) All questions are compulsory and carry equal marks.  
(2) Draw neat and well labelled diagrams wherever necessary.

## EITHER

- I. (A) Explain how decimal numbers are converted to their binary equivalent with the help of examples. Explain 1's and 2's complement method for binary subtraction with suitable example. 4+6

## OR

(B) Do as directed.

(i)  $(1010)_2 = (\text{---})_8$

(ii)  $(60)_{10} = (\text{---})_{16}$

(iii)  $(1234)_{10} = (\text{---})_{BCD}$

Explain how negative integers are represented using 2's complement number representation. Explain BCD and gray code. 3+4+3

**EITHER**

2. (A) Explain X-OR and X-NOR gates with the help of logic diagrams equations and truth tables. State and prove De'Morgan's theorems. 6+4

**OR**

- (B) Explain why NAND and NOR gates are called universal gates. Draw the logic diagram of construction of basic logic gates using NAND and NOR gates. 1+9

**EITHER**

3. (A) What is k-map ? Explain formation of pairs, quads and octets in k-map. Explain how SOP and POS equations can be converted to their standard forms. 1+6+3

**OR**

- (B) Reduce the following four variable functions using k-map also draw the logic circuit for reduced equation.  $f(A, B, C, D) = \sum m(0, 1, 2, 3, 8, 9, 10, 11)$  5+5

**EITHER**

4. (A) Explain the working of full subtracter with the help of block, logic diagrams and truth table. What is demultiplexer ? Explain 1:4 demultiplexer. 5+5

**OR**

- (B) Draw and explain half subtracter. Define encoder and decoder. Explain 4 bit Binary adder/subtractor with logic diagram. 3+2+5

5. Solve any Ten questions :—

- (a) What is the radix of hexadecimal number system ?
- (b)  $(345)_{16} = (\text{---})_2$ .
- (c) What is the 2's complement of  $(11011)_2$  ?
- (d) What is the dual of A.O. ?
- (e) Write the truth table of XNOR gate.
- (f) Draw the logic symbol of XOR gate.
- (g) What is a quad in a k-map ?
- (h) How many variables are eliminated in an octet ?
- (i) What is POS ?
- (j) What is a decoder ?
- (k) How many select lines are required for 32 input multiplexer ?
- (l) Draw a half subtractor circuit. 10x1=10