

Bachelor of Science (B.Sc.) Semester—II (C.B.S.) Examination**ELECTRONICS (SEMICONDUCTOR DEVICES)****Compulsory Paper—1**

Time : Three Hours]

[Maximum Mark : 50

Note :— (1) All questions are compulsory and carry equal marks.

(2) Draw neat diagrams wherever necessary.

EITHER

1. (A) Differentiate between BJT and FET. Explain how DE-MOSFET can be used in depletion and enhancement mode. 3+7

OR

- (B) Explain construction and working of n-channel JFET. Explain various parameters of JFET. 6+4

EITHER

2. (A) Explain construction and working of SCR. Explain its V-I characteristics.
Explain construction of UJT. Explain its use as relaxation oscillator. 5+5

OR

- (B) Explain operation of TRIAC in four different modes. Explain construction and working of DIAC. 6+4

EITHER

3. (A) Explain h-parameters. Find the following parameters of CE amplifier using h-parameters :
(i) A_i (ii) A_v (iii) Z_i . 4+6

OR

- (B) Explain class A, B and C amplifiers with the help of neat waveforms.
Explain different notations used for amplifier circuit. 6+4

EITHER

4. (A) Differentiate between voltage and power amplifiers. Explain construction and working of class B push-pull amplifier. Derive the expression for efficiency of class B amplifier. 2+5+3

OR

- (B) Explain transformer coupled class A amplifier in detail. State its advantages and disadvantages. 6+4

5. Attempt any **TEN** :—

- (a) Why FET is called as voltage controlled device ?
- (b) Draw the symbols of n-channel MOSFETs.
- (c) What is Pinch-off voltage ?
- (d) State any two applications of SCR.
- (e) Write the full forms of TRIAC and UJT.
- (f) Draw the well labelled symbols of SCR and DIAC.
- (g) What is two port network ?
- (h) What do you mean by cascading in amplifiers ?
- (i) State the uses of direct coupled amplifier.
- (j) State any two advantages of class A amplifier.
- (k) What is cross-over distortion ?
- (l) What is impedance matching in amplifiers ?

1×10=10