

**Bachelor of Science (B.Sc.) Semester—II Examination****ELECTRONICS (Semiconductor Devices)****Optional Paper—1**

Time : Three Hours]

[Maximum Marks : 50

- Note :—** (1) All questions are compulsory and carry equal marks.  
 (2) Draw neat and well labelled diagrams wherever necessary.

**EITHER**

1. (A) What is JFET ? Explain the construction and working of N-channel JFET. Give the advantages and disadvantages of FET over BJT. 1+6+3

**OR**

- (B) Explain construction of Depletion type N-channel MOSFET and explain its working with suitable diagram. Define three parameters of JFET. 7+3

**EITHER**

2. (A) What is UJT ? Explain the IV characteristics of UJT. Draw the circuit diagram of Relaxation Oscillator using UJT and explain its working. State any two applications of UJT. 5+4+1

**OR**

- (B) What is SCR ? Give the symbol of SCR. Explain the working of two transistor analogy of SCR with suitable circuit diagram. Draw and explain V-I characteristics of TRIAC. 2+5+3

**EITHER**

3. (A) What is amplifier ? Define the following amplifier parameters :

- (i) Input impedance
- (ii) Output impedance
- (iii) Voltage gain
- (iv) Current gain.

Explain classification of amplifier on the basis of Q. Point (operating point). 5+5

**OR**

- (B) Define four h-parameters of small signal CE amplifier. Draw h-parameter equivalent circuit of CE amplifier. Derive the expression for voltage gain and current gain in terms of h-parameter. 4+1+5

**EITHER**

4. (A) Explain construction and working of Class-B push-pull power amplifier. Derive an expression for its efficiency. State any two advantages of Class-B push-pull power amplifier. 3+3+3+1

**OR**

- (B) Compare voltage amplifier and power amplifier. Explain construction and working of complementary symmetry Class B power amplifier. State its any two advantages. 3+6+1

5. Solve any **TEN** :

- (A) What is MOSFET ?
- (B) State any two applications of MOSFET.
- (C) Draw transfer characteristics of JFET.
- (D) What is DIAC ?
- (E) Define the term “intrinsic stand off ratio”.
- (F) Define holding current of SCR.
- (G) Name the amplifiers on the basis of frequency.
- (H) What is DC amplifier ?
- (I) What is unit less h-parameters ?
- (J) Give any two drawbacks of Class A transformer coupled power amplifier.
- (K) What is power transistor ?
- (L) What is cross-over distortion ?

10×1=10