

**Bachelor of Science (B.Sc.) Semester—III Examination**  
**ELECTRONICS (OP-AMP & Power Supply)**  
**Optional Paper—I**

Time : Three Hours]

[Maximum Marks : 50

**Note :—** (1) **ALL** questions are compulsory and carry equal marks.

(2) Draw well labelled diagrams wherever necessary.

**EITHER**

1. (A) Compare a difference amplifier and conventional amplifier. Explain the construction and working of difference amplifier. 5+5

**OR**


- (B) Draw the block diagram of an OPAMP and Explain it. Define the terms — differential mode gain, common mode gain, CMRR, slew rate, input offset voltage with reference to OPAMP. 5+5

**EITHER**

2. (A) Compare the OPAMP as linear device and non-linear device. Explain the working of a OPAMP as Schmitt trigger. Draw the output waveforms of it, if the threshold voltage is  $\pm 2V$ . What is unity gain amplifier ? 3+5+2

**OR**

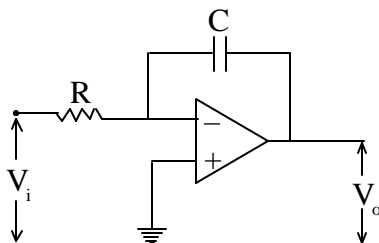
- (B) Identify the circuit and explain its working, also derive the equation for output voltage. Draw and explain the working of OPAMP circuit with input  $V_1$  given to  $R_1$ ,  $V_2$  given to  $R_2$  and  $V_3$  to  $R_3$  with feedback resistor  $R_f$ . Derive the expression for  $V_o$  if  $R_1 = R_2 = R_3 = R_f = R$ .



5+5

**EITHER**

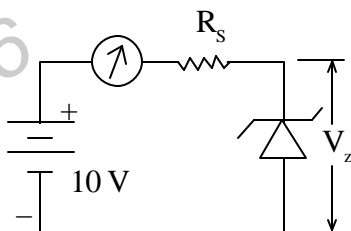3. (A) How a half wave, full wave and bridge rectifiers are different from each other ? How a zener diode is used as voltage regulator ? In given circuit, if  $V_z = 6.5 V$  calculate  $R_s$  if  $I = 75 mA$ .



6+4

**OR**

- (B) Draw the block diagram of a regulated power supply, explain its working. Define the terms — Ripple factor, efficiency, line regulation, load regulation, PIV. 5+5

**EITHER**

4. (A) Draw the block diagram and explain the working of three terminal voltage regulator. Given a transformer of 15-0-15V/50mA, draw and explain how the regulated power supply of  $\pm 12\text{V}$  using three pin IC regulators can be designed. What are the limitations of linear regulators ? 4+4+2

**OR**

- (B) State the principle of SMPS, draw and discuss the block diagram. Give its advantages and disadvantages. 10

5. Solve any **ten** :—

- (1) Can a difference amplifier amplify dc signal ?
- (2) State any two properties of an ideal OPAMP.
- (3) What is offset balancing ?
- (4) Draw circuit of a sign changer using OPAMP.
- (5) What is a zero crossing detector ?
- (6) What is differential mode gain ?
- (7) What is virtual ground concept in OPAMP ?
- (8) Give the symbol of OPAMP.
- (9) State the stability factors of a voltage regulator.
- (10) Give the drawbacks of regulated power supply.
- (11) Give pin configuration of 79XX.
- (12) What is short circuit protection ? 1×10